

My first program on D flip flop

```
// code for dff
module Dff(input d,input clk,output reg q);
    always @(posedge clk) // note: lines within the always block are executed sequentially
    begin
        q<=d;
    end
endmodule
// code ends
```

D flip flop as we all know is a one bit storage device and its used to model sequential circuits.

REGISTER

Few d flip flops can be used as an array to create a register. Well u can directly use the data type "reg" but i provide this code as its explains the use of structural coding . You can alter the size of the register to increase the size for the code below

```
//code for
module reg4(input [3:0] d,input clk,output [3:0] q);
    Dff r1(d[0],clk,q[0]); // this process of calling a module is called instantiating
    Dff r2(d[1],clk,q[1]);
    Dff r3(d[2],clk,q[2]);
    Dff r4(d[3],clk,q[3]);
endmodule
// code ends
```

Traffic light controller using task

```
// code foe traffic light controller
module traffic_lights;
    reg clock, red, amber, green;
    parameter on = 1, off = 0, red_tics = 30,
        amber_tics = 3, green_tics = 20;

    initial red = off;
    initial amber = off;
    initial green = off;

    always begin // sequence to control the lights.
        red = on; // turn red light on
        light(red, red_tics); // and wait.
```

```

green = on; // turn green light on
light(green, green_tics); // and wait.
amber = on; // turn amber light on
light(amber, amber_tics); // and wait.
end
// task to wait for tics positive edge clocks
// before turning color light off.
task light;
output color;
input [31:0] tics;
begin
repeat (tics) @ (posedge clock);
color = off; // turn light off.
end
endtask

always begin // waveform for the clock.
#10 clock = 0;
#10 clock = 1;
end
endmodule // traffic_lights.
// code ends

```

32 bit booth multiplier

```

module mul32(x,y,z);
    input signed[31:0] x;
    input signed[31:0] y;
    output signed [63:0] z;
    reg signed[63:0] z;
    reg [1:0] temp;
    reg e;
    reg [31:0] y1;
    integer i;
    always@(x,y)
    begin
        e=1'd0;
        z=64'd0;
        for(i=0;i<32; i=i+1)&lt;/font">
            begin
                temp={x[i],e};
                y1=-y;

```

```

case(temp)
2'd2:z[63:32]=z[63:32]+y1;
2'd1:z[63:32]=z[63:32]+y;
default:begin
end

endcase
z=z &gt;&gt;1;
z[63]=z[62];
e=x[i];
end
if(y==32'd2147483648)
    z=-z;
end
endmodule

```

32 bit carry look ahead adder

```

// code starts here
module cla32( d1,d2,clk,cin,sum,cout);
    input [31:0] d1;
    input [31:0] d2;
    input clk;
    input cin;
    output cout;
    output [31:0] sum;

    wire c0,c1,c2,c3,c4,c5,c6;
    reg [31:0] b;
    always@(posedge clk)
    begin
        if(cin==1)
            b<=-d2-1;
        else
            b<=d2;
        end
        cla4 n1(d1[3:0],b[3:0],clk,cin,sum[3:0],c0);
        cla4 n2(d1[7:4],b[7:4],clk,c0,sum[7:4],c1);
        cla4 n3(d1[11:8],b[11:8],clk,c1,sum[11:8],c2);
        cla4 n4(d1[15:12],b[15:12],clk,c2,sum[15:12],c3);
        cla4 n5(d1[19:16],b[19:16],clk,c3,sum[19:16],c4);
        cla4 n6(d1[23:20],b[23:20],clk,c4,sum[23:20],c5);
    end
endmodule

```

```
cla4 n7(d1[27:24],b[27:24],clk,c5,sum[27:24],c6);
cla4 n8(d1[31:28],b[31:28],clk,c6,sum[31:28],cout);
endmodule
```

//clad 4 module

```
module cla4(a,b,cin,s,cout);
input[3:0] a,b;
input cin;
output cout;
output[3:0] s;
wire[3:0] g,p;
wire[13:0] z;
```

```
xor21 x1 (.a1(a[0]),.a2(b[0]),.z(p[0]));
and21 x2 (.a1(a[0]),.a2(b[0]),.z(g[0]));
xor21 x3 (.a1(a[1]),.a2(b[1]),.z(p[1]));
and21 x4 (.a1(a[1]),.a2(b[1]),.z(g[1]));
xor21 x5 (.a1(a[2]),.a2(b[2]),.z(p[2]));
and21 x6 (.a1(a[2]),.a2(b[2]),.z(g[2]));
xor21 x7 (.a1(a[3]),.a2(b[3]),.z(p[3]));
and21 x8 (.a1(a[3]),.a2(b[3]),.z(g[3]));
```

```
xor21 x9 (.a1(cin),.a2(p[0]),.z(s[0]));
and21 x10 (.a1(cin),.a2(p[0]),.z(z[0]));
or21 x11 (.a1(z[0]),.a2(g[0]),.z(z[1]));
xor21 x12 (.a1(z[1]),.a2(p[1]),.z(s[1]));
```

```
and31 x13 (.a1(cin),.a2(p[0]),.a3(p[1]),.z(z[2]));
and21 x14 (.a1(g[0]),.a2(p[1]),.z(z[3]));
or31 x15 (.a1(z[2]),.a2(z[3]),.a3(g[1]),.z(z[4]));
xor21 x16 (.a1(z[4]),.a2(p[2]),.z(s[2]));
```

```
and41 x17 (.a1(cin),.a2(p[0]),.a3(p[1]),.a4(p[2]),.z(z[5]));
and31 x18 (.a1(g[0]),.a2(p[1]),.a3(p[2]),.z(z[6]));
and21 x19 (.a1(g[1]),.a2(p[2]),.z(z[7]));
or41 x20 (.a1(z[5]),.a2(z[6]),.a3(z[7]),.a4(g[2]),.z(z[8]));
xor21 x21 (.a1(z[8]),.a2(p[3]),.z(s[3]));
```

```
and41 x22 (.a1(cin),.a2(p[0]),.a3(p[1]),.a4(p[2]),.z(z[9]));
and31 x23 (.a1(g[0]),.a2(p[1]),.a3(p[2]),.z(z[10]));
and21 x24 (.a1(g[1]),.a2(p[2]),.z(z[11]));
or41 x25 (.a1(z[9]),.a2(z[10]),.a3(z[11]),.a4(g[2]),.z(z[12]));
and21 x26 (.a1(z[12]),.a2(p[3]),.z(z[13]));
```

```
or21 x27 (.a1(z[13]),.a2(g[3]),.z(cout));
endmodule
```

```
//xor
module xor21(a1,a2,z);
input a1,a2; output z;
reg z;
always@(a1,a2)
begin
z<=a1 ^ a2;
end
endmodule
```

```
//and
module and21(
a1,
a2,
z
);
input a1;
input a2;
output z;
assign z=a1&a2;
endmodule
```

```
//or
module or21(a1,a2,z);
input a1,a2; output z;
reg z;
always@(a1,a2)
begin
z<=a1 | a2;
end
endmodule
```

```
module or31(a1,a2,a3,z);
input a1,a2,a3; output z;
reg z;
always@(a1,a2,a3)
begin
z<=a1 | a2 | a3;
end
```

```

endmodule

module or41(a1,a2,a3,a4,z);
input a1,a2,a3,a4; output z;
reg z;
always@(a1,a2,a3,a4)
begin
z<=a1 | a2 | a3 | a4;
end
endmodule

//code ends here

```

DSP Butterfly unit

```

//code starts here
module butterfly(
ar,
ai,
// ar+jai is the first number
br,
bi,
// br+jbi is the second number
wr,
wi,
// wr+jwi is the twiddle factor
z1r,
z1i,
z2r,
z2i,
clk,

z1r_c,
z1i_c,
z2r_c,
z2i_c

);

input [31:0]ar,ai,br,bi;
input [32:0]wr,wi;
input clk;

```

```

output[31:0] z1r,z1i,z2r,z2i,z1r_c,z1i_c,z2r_c,z2i_c;

wire [31:0] x1,x2,x3,x4,z_t_i,z_t_i_c,z_t_r,z_t_r_c;

// multliper stage-4
mul32 s1(br,wr,x1);
mul32 s2(bi,wi,x2);
mul32 s3(br,wi,x3);
mul32 s4(bi,wr,x4);
//adder stage-6
cla32 s5(x3,x4,clk,0,z_t_i,z_t_i_c);//temp2
cla32 s6(x1,x2,clk,1,z_t_r,z_t_r_c);//temp1

cla32 s7(z_t_r,ar,clk,0,z1r,z1r_c);
cla32 s8(z_t_i,ai,clk,0,z1i,z1i_c);

cla32 s9(ar,z_t_r,clk,1,z2r,z2r_c);
cla32 s10(ai,z_t_i,clk,1,z2i,z2i_c);

endmodule
// code ends here

```

HALF ADDER

```

module
halfadder(a,b,sum,carry);
input a,b;
output sum, carry;
wire sum, carry;
assign sum = a^b; // sum bit
assign carry = (a& b);
//carry bit
endmodule

```

FULL ADDER

```

module fulladder(a,b,c,sum,carry);
input a,b,c;
output sum,carry;

```

```

wire sum,carry;
assign sum=a^b^c; // sum bit
assign carry=((a&amp;b) | (b&amp;c) | (a&amp;c)); //carry bit
endmodule

```

JK FLIP FLOP

```

`define TICK #2 //Flip-flop time delay 2 units
module jkflop(j,k,clk,rst,q);
input j,k,clk,rst;
output q;
reg q;
always @(posedge clk)begin
if(j==1 &amp; k==1 &amp; rst==0)begin
q &lt;=`TICK ~q; //Toggles
end
else if(j==1 &amp; k==0 &amp; rst==0)begin
q &lt;=`TICK 1; //Set
end
else if(j==0 &amp; k==1)begin
q &lt;=`TICK 0; //Cleared
end
end
always @(posedge rst)begin
q &lt;= 0; //The reset normally has negligible delay and hence ignored.
end

endmodule

```

VEDIC MULTIPLIER

Indians have always proved that it has a great history of great mathematicians . Vedic maths is one of the discovery of Indians. One i read one such algorithm i decided to code one such algorithm and check for its speed and compare it with normal conventional multipliers. Here is a code for a 2 bit vedic multiplier

```

// code starts here
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer: Somshekhar R Puranmath

```



```

// Module Name:  vedic_2_x_2
// Target Devices: spartan 6
// Tool versions: Xilinx 13.3
/////////////////////////////////////////////////////////////////
module vedic_2_x_2(
a,
b,
c

);
input [1:0]a;// first input
input [1:0]b;// second input
output [3:0]c;// output
wire [3:0]c;
wire [3:0]temp;
// four multiplication operation of bits according to vedic logic
assign c[0]=a[0]&and;b[0];
assign temp[0]=a[1]&and;b[0];
assign temp[1]=a[0]&and;b[1];
assign temp[2]=a[1]&and;b[1];
// using two half adders
ha z1(temp[0],temp[1],c[1],temp[3]);
ha z2(temp[2],temp[3],c[2],c[3]);
endmodule


```

```

//code for Half adder
module ha(a, b, sum, carry);
// a and b are inputs
input a;
input b;
output sum;
output carry;
assign carry=a&and;b;
assign sum=a^b;
endmodule
// code ends

```

 The above algorithm is according to the **URDHVA TIRYAKBHYAM SUTRA**. Here is a image illustrating the algorithm



2:4 decoder

// code starts here

```
module dec2_4 (a,b,en,y0,y1,y2,y3)
```

```
input a, b, en;
```

```
output y0,y1,y2,y3;
```

```
assign y0= (~a) && (~b) && en;
```

```
assign y1= (~a) && b && en;
```

```
assign y2= a && (~ b) && en;
```

```
assign y3= a && b && en;
```

```
end module
```

```
// code
```

ends

8:3 encoder with priority

//code starts here

```
module enc8_3 (I, en, y, v);
```

```
input [7:0]I;
```

```
input en;
```

```
output v;
```

```
output [2:0]y;
```

```
sig y; sig v;
```

```
always @ (en, I)
```

```
begin
```

```
if(en= =0)
```

```

        v=0;
    else
        v=1;
    end
    if ( I[7]= 1 & & en= 1)          y=3'b111;
    else if ( I[6]==1 & & en==1)    y=3'b110;
    else if ( I[5]==1 & & en==1)    y=3'b101;
    else if ( I[4]==1 & & en==1)    y=3'b100;
    else if ( I[3]==1 & & en==1)    y=3'b011;
    else if ( I[2]==1 & & en==1)    y=3'b010;
    else if ( I[1]==1 & & en==1)    y=3'b001;
    else if ( I[0]==1 & & en==1)    y=3'b000;
    else y=3'b000;
    end
endmodule
// code ends here

```

8 TO 1 MULTIPLEXER

//code starts here

```

module mux8_1
input [7:0]I;
output [2:0]S;
output y;
input en;
reg y;
always @(en,S,I,y);
begin
    if (en= 1)
    begin
        if (s= 000 y=I[0];
        else if (s==001) y=I[1];
        else if (s==001) y=I[2];
        else if (s==001) y=I[3];
        else if (s==001) y=I[4];
        else if (s==001) y=I[5];
        else if (s==001) y=I[6];
        else if (s==001) y=I[7];
    end
    else y=0;
end

```

```
end
end
endmodule
//code
```

ends

4-BIT BINARY TO GRAY COUNTER CONVERTER

```
//code starts here
module b2g(b,g);
input [3:0] b;
output [3:0] g;
xor (g[0],b[0],b[1]),
    (g[1],b[1],b[2]),
    (g[2],b[2],b[3]);
assign g[3]=b[3];
endmodule
//code ends
```

DE-MULTIPLEXER (1 TO 4)

```
//code starts here
module demux (s2,s1,I,en,y0,y1,y2,y3)
input s2,s1,I,en;
output y0,y1,y2,y3;
assign y0=(~s2)&&(~s1)&& I&& en;
assign y1=(~s2)&& s1&& I&& en;
assign y2=s2&&(~s1)&& I && en;
assign y3=s2&& s1 && I && en;
endmodule
//code ends
```

SR FLIPFLOP

```
module srff(s,r,clk,rst, q,qb);
input s,r,clk,rst;
output q,qb;
reg q,qb;
reg [1:0]sr;
always@(posedge clk,posedge rst)
```

```

begin
  sr={s,r};
  if(rst==0)
    begin
      case (sr)
        2'd1:q=1'b0;
        2'd2:q=1'b1;
        2'd3:q=1'b1;
        default: begin end
      endcase
    end
  else
    begin
      q=1'b0;
      end

      qb=~q;
      end

endmodule

```

BINARY 4 bit COUNTER(UP/DOWN)

```

module bin_as(clk,clr,dir, temp);
  input clk,clr,dir;
  output reg[3:0] temp;
  always@(posedge clk,posedge clr)
    begin
      if(clr==0)
        begin
          if(dir==0)
            temp=temp+1;
          else temp=temp-1;
          end
        else
          temp=4'd0;
          end
    end
endmodule

```

Linear feed back shift register (8 bit)

```
module lfsr      (
  out            , // Output of the counter
  enable        , // Enable  for counter
  clk           , // clock input
  reset         , // reset input
);

//-----Output Ports-----
output [7:0] out;
//-----Input Ports-----
input [7:0] data;
input enable, clk, reset;
//-----Internal Variables-----
reg [7:0] out;
wire      linear_feedback;

//-----Code Starts Here-----
assign linear_feedback = !(out[7] ^ out[3]);

always @(posedge clk)
if (reset) begin // active high reset
  out &lt;= 8'b0 ;
end else if (enable) begin
  out &lt;= {out[6],out[5],
          out[4],out[3],
          out[2],out[1],
          out[0], linear_feedback};
end

endmodule // End Of Module counter
```

Grey counter

```
module gray_counter (
  out      , // counter out
  enable   , // enable for counter
  clk      , // clock
  rst      , // active hight reset
);

//-----Input Ports-----
input clk, rst, enable;
//-----Output Ports-----
output [ 7:0] out;
//-----Internal Variables-----
wire [7:0] out;
reg [7:0] count;
//-----Code Starts Here-----
always @ (posedge clk)
if (rst)
  count &lt;= 0;
else if (enable)
  count &lt;= count + 1;

assign out = { count[7], (count[7] ^ count[6]), (count[6] ^
```

```

count[5]), (count[5] ^ count[4]), (count[4] ^
count[3]), (count[3] ^ count[2]), (count[2] ^
count[1]), (count[1] ^ count[0]) };

```

```
endmodule
```

UART

```

module uart (
reset
,
txclk
,
ld_tx_data
,
tx_data
,
tx_enable
,
tx_out
,
tx_empty
,
rxclk
,
uld_rx_data
,
rx_data
,
rx_enable
,
rx_in
,
rx_empty
);
// Port declarations
input      reset      ;
input      txclk       ;
input      ld_tx_data  ;
input [7:0] tx_data    ;
input      tx_enable   ;
output     tx_out      ;
output     tx_empty    ;
input      rxclk       ;
input      uld_rx_data ;
output [7:0] rx_data    ;
input      rx_enable   ;
input      rx_in       ;
output     rx_empty    ;

// Internal Variables
reg [7:0] tx_reg      ;
reg      tx_empty     ;
reg      tx_over_run  ;
reg [3:0] tx_cnt      ;
reg      tx_out       ;
reg [7:0] rx_reg      ;
reg [7:0] rx_data     ;
reg [3:0] rx_sample_cnt ;
reg [3:0] rx_cnt      ;
reg      rx_frame_err ;
reg      rx_over_run  ;
reg      rx_empty     ;
reg      rx_d1        ;
reg      rx_d2        ;
reg      rx_busy      ;

```

```

// UART RX Logic
always @ (posedge rxclk or posedge reset)
if (reset) begin
    rx_reg        &lt;= 0;
    rx_data        &lt;= 0;
    rx_sample_cnt  &lt;= 0;
    rx_cnt         &lt;= 0;
    rx_frame_err   &lt;= 0;
    rx_over_run    &lt;= 0;
    rx_empty       &lt;= 1;
    rx_d1          &lt;= 1;
    rx_d2          &lt;= 1;
    rx_busy        &lt;= 0;
end else begin
    // Synchronize the asynch signal
    rx_d1 &lt;= rx_in;
    rx_d2 &lt;= rx_d1;
    // Uload the rx data
    if (uld_rx_data) begin
        rx_data &lt;= rx_reg;
        rx_empty &lt;= 1;
    end
    // Receive data only when rx is enabled
    if (rx_enable) begin
        // Check if just received start of frame
        if (!rx_busy & & & !rx_d2) begin
            rx_busy        &lt;= 1;
            rx_sample_cnt  &lt;= 1;
            rx_cnt         &lt;= 0;
        end
        // Start of frame detected, Proceed with rest of data
        if (rx_busy) begin
            rx_sample_cnt &lt;= rx_sample_cnt + 1;
            // Logic to sample at middle of data
            if (rx_sample_cnt == 7) begin
                if ((rx_d2 == 1) & & & (rx_cnt == 0)) begin
                    rx_busy &lt;= 0;
                end else begin
                    rx_cnt &lt;= rx_cnt + 1;
                    // Start storing the rx data
                    if (rx_cnt &gt; 0 & & & rx_cnt &lt; 9) begin
                        rx_reg[rx_cnt - 1] &lt;= rx_d2;
                    end
                    if (rx_cnt == 9) begin
                        rx_busy &lt;= 0;
                        // Check if End of frame received correctly
                        if (rx_d2 == 0) begin
                            rx_frame_err &lt;= 1;
                        end else begin
                            rx_empty &lt;= 0;
                            rx_frame_err &lt;= 0;
                            // Check if last rx data was not unloaded,
                            rx_over_run &lt;= (rx_empty) ? 0 : 1;
                        end
                    end
                end
            end
        end
    end
end
end

```



```

        end
    end
end
if (!rx_enable) begin
    rx_busy &lt;= 0;
end
end

// UART TX Logic
always @ (posedge txclk or posedge reset)
if (reset) begin
    tx_reg      &lt;= 0;
    tx_empty    &lt;= 1;
    tx_over_run &lt;= 0;
    tx_out      &lt;= 1;
    tx_cnt      &lt;= 0;
end else begin
    if (ld_tx_data) begin
        if (!tx_empty) begin
            tx_over_run &lt;= 0;
        end else begin
            tx_reg &lt;= tx_data;
            tx_empty &lt;= 0;
        end
    end
    if (tx_enable & & & !tx_empty) begin
        tx_cnt &lt;= tx_cnt + 1;
        if (tx_cnt == 0) begin
            tx_out &lt;= 0;
        end
        if (tx_cnt &gt; 0 & & & tx_cnt &lt; 9) begin
            tx_out &lt;= tx_reg[tx_cnt - 1];
        end
        if (tx_cnt == 9) begin
            tx_out &lt;= 1;
            tx_cnt &lt;= 0;
            tx_empty &lt;= 1;
        end
    end
    if (!tx_enable) begin
        tx_cnt &lt;= 0;
    end
end

endmodule

```

Arbiter implemented with 4 requests

```

module fsm_full(

```

```

clock , // Clock
reset , // Active high reset
req_0 , // Active high request from agent 0
req_1 , // Active high request from agent 1
req_2 , // Active high request from agent 2
req_3 , // Active high request from agent 3
gnt_0 , // Active high grant to agent 0
gnt_1 , // Active high grant to agent 1
gnt_2 , // Active high grant to agent 2
gnt_3 // Active high grant to agent 3
);
// Port declaration here
input clock ; // Clock
input reset ; // Active high reset
input req_0 ; // Active high request from agent 0
input req_1 ; // Active high request from agent 1
input req_2 ; // Active high request from agent 2
input req_3 ; // Active high request from agent 3
output gnt_0 ; // Active high grant to agent 0
output gnt_1 ; // Active high grant to agent 1
output gnt_2 ; // Active high grant to agent 2
output gnt_3 ; // Active high grant to agent

// Internal Variables
reg    gnt_0 ; // Active high grant to agent 0
reg    gnt_1 ; // Active high grant to agent 1
reg    gnt_2 ; // Active high grant to agent 2
reg    gnt_3 ; // Active high grant to agent

parameter [2:0] IDLE  = 3'b000;
parameter [2:0] GNT0  = 3'b001;
parameter [2:0] GNT1  = 3'b010;
parameter [2:0] GNT2  = 3'b011;
parameter [2:0] GNT3  = 3'b100;

reg [2:0] state, next_state;

always @ (state or req_0 or req_1 or req_2 or req_3)
begin
    next_state = 0;
    case(state)
        IDLE : if (req_0 == 1'b1) begin
            next_state = GNT0;
        end else if (req_1 == 1'b1) begin
            next_state= GNT1;
        end else if (req_2 == 1'b1) begin
            next_state= GNT2;
        end else if (req_3 == 1'b1) begin
            next_state= GNT3;
        end else begin
            next_state = IDLE;
        end
        GNT0 : if (req_0 == 1'b0) begin
            next_state = IDLE;
        end else begin
            next_state = GNT0;
        end
    end
end

```

```

        GNT1 : if (req_1 == 1'b0) begin
            next_state = IDLE;
        end else begin
            next_state = GNT1;
        end
        GNT2 : if (req_2 == 1'b0) begin
            next_state = IDLE;
        end else begin
            next_state = GNT2;
        end
        GNT3 : if (req_3 == 1'b0) begin
            next_state = IDLE;
        end else begin
            next_state = GNT3;
        end
        default : next_state = IDLE;
    endcase
end

always @ (posedge clock)
begin : OUTPUT_LOGIC
    if (reset) begin
        gnt_0 &lt;= #1 1'b0;
        gnt_1 &lt;= #1 1'b0;
        gnt_2 &lt;= #1 1'b0;
        gnt_3 &lt;= #1 1'b0;
        state &lt;= #1 IDLE;
    end else begin
        state &lt;= #1 next_state;
        case(state)
        IDLE : begin
            gnt_0 &lt;= #1 1'b0;
            gnt_1 &lt;= #1 1'b0;
            gnt_2 &lt;= #1 1'b0;
            gnt_3 &lt;= #1 1'b0;

            end
        GNT0 : begin
            gnt_0 &lt;= #1 1'b1;
            end
        GNT1 : begin
            gnt_1 &lt;= #1 1'b1;
            end
        GNT2 : begin
            gnt_2 &lt;= #1 1'b1;
            end
        GNT3 : begin
            gnt_3 &lt;= #1 1'b1;
            end
        default : begin
            state &lt;= #1 IDLE;
            end
        endcase
    end
end
endmodule

```

Memory design -ram/rom

Ram

```
module ram1(clk,enable,rdwr,address,dtin,dtout);
```

```
//parameter N=10;
```

```
input clk,enable,rdwr;
```

```
input[9:0] address;
```

```
input[15:0] dtin;
```

```
output [15:0] dtout;
```

```
reg[15:0] dtout;
```

```
reg[15:0] memory[0:1023];
```

```
//reg[15:0] mem;
```

```
always@(posedge clk)
```

```
begin
```

```
if(enable==1'b1)
```

```
begin
```

```
if(rdwr==1'b0)
```

```
begin
```

```
memory[address]&lt;=dtin;
```

```
end
```

```

else

dtout<= memory[address];

end

else

dtout<=16'bz;

end

endmodule

```

Rom

```

module rom1(clk,romrd,address,dtout);

parameter N=8; input[N-2:0] address;

input clk,romrd; output[15:0] dtout;

reg[15:0] dtout; reg[15:0] romarray[0:(2**N-1)-1];

always@(posedge clk)

begin romarray[0]=16'b0111111111111111;

romarray[1]=16'b0111011001000010;

romarray[2]=16'b0101101010000010;

romarray[3]=16'b0011000011111100;

romarray[4]=16'b0000000000000000;

```

```

romarray[5]=16'b1100111100000100;

romarray[6]=16'b1010010101111110;

romarray[7]=16'b1000100110111110; //real twiddle factors

if(romrd==1)

begin

dtout&lt;=romarray[address];

end else

dtout&lt;=16'bz;

end

endmodule

```

Fibonacci number generator

```

module fibNumberGenNE(startingValue, fibNum);
    input  [15:0] startingValue;
    output [15:0] fibNum;

    reg [15:0] myValue;
    reg [15:0] fibNum;

    always
    begin
        @ng.ready //accept event signal
            myValue = startingValue;
        for (fibNum = 0; myValue != 0; myValue = myValue - 1)
            fibNum = fibNum + myValue;
        $display ("%d, fibNum=%d", $time, fibNum);
    end
endmodule

```

RS232 transmitter

```

module RS232_Transmitter (
    clock,
    reset_neg,
    tx_datain_ready,
    Present_Processing_Completed,
    tx_datain,
    tx_transmitter,
    tx_transmitter_valid
);

    parameter HIGH = 1'b1;
    parameter LOW  = 1'b0;

    parameter CLOCK_FREQ = 100000000; // 100MHz
    // parameter CLOCK_FREQ = 33000000; // 33MHz

    parameter BAUD_RATE = 115200; // ;9600

    parameter REG_INPUT = 1; // in REG_INPUT mode, the input doesn't have to
    stay valid while the character is been transmitted

    parameter BAUD_ACC_WIDTH = 16;

    input reset_neg;
    input clock;
    input tx_datain_ready;
    input Present_Processing_Completed;
    input [7:0] tx_datain;
    output tx_transmitter;
    output tx_transmitter_valid;

    reg tx_transmitter;

    // Baud generator
    wire [BAUD_ACC_WIDTH:0] Baun_Inc;
    reg [BAUD_ACC_WIDTH:0] Baud_Acc;

    assign Baun_Inc = ((BAUD_RATE << (BAUD_ACC_WIDTH - 4)) + (CLOCK_FREQ >> 5))
        / (CLOCK_FREQ >> 4);

    wire Baud_Pulse = Baud_Acc[BAUD_ACC_WIDTH];

    always @ (posedge clock or negedge reset_neg)
    begin
        if (reset_neg == LOW)
            begin
                Baud_Acc <= {(BAUD_ACC_WIDTH + 1){LOW}};
            end
        else if (Present_Processing_Completed == 1'b1) Baud_Acc <=
        {(BAUD_ACC_WIDTH + 1){LOW}};
        else if (tx_transmitter_valid)
            begin
                Baud_Acc <= Baud_Acc[BAUD_ACC_WIDTH - 1:0] + Baun_Inc;
            end
    end
end

```

```

// Transmitter State machine
reg [3:0] State;
wire tx_Xfer_Ready = (State==0);
assign tx_transmitter_valid = ~tx_Xfer_Ready;

reg [7:0] tx_data_reg;
always @ (posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        tx_data_reg <= 8'hff;
    end
    else if (Present_Processing_Completed == 1'b1) tx_data_reg <= 8'hff;
    else if (tx_Xfer_Ready & tx_datain_ready)
    begin
        tx_data_reg <= tx_datain;
    end
end

    wire [7:0] Tx_Data_Byte;

assign Tx_Data_Byte = REG_INPUT ? tx_data_reg : tx_datain;

always @ (posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        State <= 4'b0000;
    end
    else if (Present_Processing_Completed == 1'b1) State <= 4'b0000;
    else
    begin
        case(State)
            4'b0000: if(tx_datain_ready) State <= 4'b0100;
            // 4'b0001: if(Baud_Pulse) State <= 4'b0100; // registered input
            4'b0100: if(Baud_Pulse) State <= 4'b1000; // start
            4'b1000: if(Baud_Pulse) State <= 4'b1001; // bit 0
            4'b1001: if(Baud_Pulse) State <= 4'b1010; // bit 1
            4'b1010: if(Baud_Pulse) State <= 4'b1011; // bit 2
            4'b1011: if(Baud_Pulse) State <= 4'b1100; // bit 3
            4'b1100: if(Baud_Pulse) State <= 4'b1101; // bit 4
            4'b1101: if(Baud_Pulse) State <= 4'b1110; // bit 5
            4'b1110: if(Baud_Pulse) State <= 4'b1111; // bit 6
            4'b1111: if(Baud_Pulse) State <= 4'b0010; // bit 7
            4'b0010: if(Baud_Pulse) State <= 4'b0000; // stop1
            // 4'b0011: if(Baud_Pulse) State <= 4'b0000; // stop2
            default: if(Baud_Pulse) State <= 4'b0000;
        endcase
    end
end

// Output mux
reg MuxBit;

always @ (State or Tx_Data_Byte)
begin
    case (State[2:0])

```



```

        3'd0: MuxBit <= Tx_Data_Byte[0];
        3'd1: MuxBit <= Tx_Data_Byte[1];
        3'd2: MuxBit <= Tx_Data_Byte[2];
        3'd3: MuxBit <= Tx_Data_Byte[3];
        3'd4: MuxBit <= Tx_Data_Byte[4];
        3'd5: MuxBit <= Tx_Data_Byte[5];
        3'd6: MuxBit <= Tx_Data_Byte[6];
        3'd7: MuxBit <= Tx_Data_Byte[7];
    endcase
end

// Put together the start, data and stop bits
always @ (posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        tx_transmitter <= HIGH;
    end
    else if (Present_Processing_Completed == 1'b1) tx_transmitter <= HIGH;
    else
    begin
        tx_transmitter <= (State < 4) | (State[3] & MuxBit); // register the
        output to make it glitch free
    end
end

endmodule

```

RS232 receiver

```

module RS232_Receiver (
    reset_neg,
    clock,
    rx_receiver,
    rx_dataout_ready,
    rx_dataout,

    // optional pins for identifying long break in data reception
    rx_endofpacket,
    rx_Idle,
    Exe_LogicImp
);

    parameter HIGH = 1'b1;
    parameter LOW  = 1'b0;

    //`ifndef ML401
        parameter CLOCK_FREQ = 100000000; // 100MHz
    //`else // ifdef ML461
        parameter CLOCK_FREQ = 33000000; // 33MHz
    //`endif

    //parameter BAUD_RATE = 9600; // 115200;
    parameter BAUD_RATE = 115200; // 115200;

    // BAUD_RATE generator (Uses 8 times oversampling)
    parameter BAUD_RATE_8X = BAUD_RATE*8;

```

```

parameter BAUD_8X_ACC_WIDTH = 16;

input reset_neg;
input clock;
input rx_receiver;
input Exe_LogicImp;
output rx_dataout_ready;
output [7:0] rx_dataout;

// optional pins for identifying long break in data reception
// We also detect if a gap occurs in the received stream of characters
// That can be useful if multiple characters are sent in burst
// so that multiple characters can be treated as a "packet"
output rx_endofpacket; // one clock pulse, when no more data
                        // is received (rx_Idle is going high)
output rx_Idle; // no data is being received

wire [BAUD_8X_ACC_WIDTH:0] Baud_8X_Incr;
reg [BAUD_8X_ACC_WIDTH:0] Baud_8X_Acc;

assign Baud_8X_Incr = ((BAUD_RATE_8X << (BAUD_8X_ACC_WIDTH - 7)) +
(CLOCK_FREQ >> 8))
                        / (CLOCK_FREQ >> 7);

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        Baud_8X_Acc <= {(BAUD_8X_ACC_WIDTH + 1){LOW}};
    end
    else if (Exe_LogicImp == 1'b1) Baud_8X_Acc <= {(BAUD_8X_ACC_WIDTH +
1){LOW}};
    else
    begin
        Baud_8X_Acc <= Baud_8X_Acc[BAUD_8X_ACC_WIDTH - 1:0]
                        + Baud_8X_Incr;
    end
end
wire Baud_Pulse_8x = Baud_8X_Acc[BAUD_8X_ACC_WIDTH];

////////////////////////////////////
reg [1:0] Rx_Sync;

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        Rx_Sync <= 2'b11;
    end
    else if (Exe_LogicImp == 1'b1) Rx_Sync <= 2'b11;
    else if (Baud_Pulse_8x)
    begin
        Rx_Sync <= {Rx_Sync[0], rx_receiver};
    end
end

reg [1:0] Rx_Count;

```

```

    reg Rx_Bit;

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        Rx_Count <= 2'b11;
        Rx_Bit <= HIGH;
    end
    else if (Exe_LogicImp == 1'b1)
    begin
        Rx_Count <= 2'b11;
        Rx_Bit <= HIGH;
    end
    else if (Baud_Pulse_8x)
    begin
        if( Rx_Sync[1] && Rx_Count!=2'b11) Rx_Count <= Rx_Count + 2'h1;
        else
        if(~Rx_Sync[1] && Rx_Count!=2'b00) Rx_Count <= Rx_Count - 2'h1;

        if(Rx_Count==2'b00) Rx_Bit <= 1'b0;
        else
        if(Rx_Count==2'b11) Rx_Bit <= 1'b1;
    end
end

    reg [3:0] State;
    reg [3:0] Bit_Spacing;

    // "next_bit" controls when the data sampling occurs
    // depending on how noisy the rx_receiver is, different values might work
better
    // with a clean connection, values from 8 to 11 work
    wire next_bit = (Bit_Spacing==4'd10);

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        Bit_Spacing <= 4'b0000;
    end
    else if (Exe_LogicImp == 1'b1) Bit_Spacing <= 4'b0000;
    else if (State==0)
    begin
        Bit_Spacing <= 4'b0000;
    end
    else if (Baud_Pulse_8x)
    begin
        Bit_Spacing <= {Bit_Spacing[2:0] + 4'b0001} | {Bit_Spacing[3], 3'b000};
    end
end

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        State <= 4'b0000;
    end
end

```

```

end
else if (Exe_LogicImp == 1'b1)  State <= 4'b0000;
else if (Baud_Pulse_8x)
begin
case(State)
4'b0000: if(~Rx_Bit) State <= 4'b1000;  // start bit found?
4'b1000: if(next_bit) State <= 4'b1001;  // bit 0
4'b1001: if(next_bit) State <= 4'b1010;  // bit 1
4'b1010: if(next_bit) State <= 4'b1011;  // bit 2
4'b1011: if(next_bit) State <= 4'b1100;  // bit 3
4'b1100: if(next_bit) State <= 4'b1101;  // bit 4
4'b1101: if(next_bit) State <= 4'b1110;  // bit 5
4'b1110: if(next_bit) State <= 4'b1111;  // bit 6
4'b1111: if(next_bit) State <= 4'b0001;  // bit 7
4'b0001: if(next_bit) State <= 4'b0000;  // stop bit
default: State <= 4'b0000;
endcase
end
end

reg [7:0] rx_dataout;

always @(posedge clock or negedge reset_neg)
begin
if (reset_neg == LOW)
begin
rx_dataout <= 8'h00;
end
else if (Exe_LogicImp == 1'b1) rx_dataout <= 8'h00;
else if (Baud_Pulse_8x && next_bit && State[3])
begin
rx_dataout <= {Rx_Bit, rx_dataout[7:1]};
end
end

reg rx_dataout_ready, RxD_data_error;

always @(posedge clock or negedge reset_neg)
begin
if (reset_neg == LOW)
begin
rx_dataout_ready <= LOW;
RxD_data_error <= LOW;
end
else if (Exe_LogicImp == 1'b1)
begin
rx_dataout_ready <= LOW;
RxD_data_error <= LOW;
end
else
begin
rx_dataout_ready <= (Baud_Pulse_8x && next_bit && State==4'b0001 &&
Rx_Bit);  // ready only if the stop bit is received
RxD_data_error <= (Baud_Pulse_8x && next_bit && State==4'b0001 &&
~Rx_Bit);  // error if the stop bit is not received
end
end
end

```

```

// Optional functionality for detection of gap if it occurs in the
// received stream of characters.
    reg [4:0] gap_count;

always @ (posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        gap_count<=5'h00;
    end
    else if (Exe_LogicImp == 1'b1) gap_count<=5'h00;
    else if (State!=0)
    begin
        gap_count<=5'h00;
    end
    else if (Baud_Pulse_8x & ~gap_count[4])
    begin
        gap_count <= gap_count + 5'h01;
    end
end

assign rx_Idle = gap_count[4];

    reg rx_endofpacket;

always @(posedge clock or negedge reset_neg)
begin
    if (reset_neg == LOW)
    begin
        rx_endofpacket <= LOW;
    end
    else if (Exe_LogicImp == 1'b1) rx_endofpacket <= LOW;
    else
    begin
        rx_endofpacket <= Baud_Pulse_8x & (gap_count==5'h0F);
    end
end

endmodule

```

Bcd to binary conversion

```

module bcd_to_binary (
    clk_i,
    ce_i,
    rst_i,
    start_i,
    dat_bcd_i,
    dat_binary_o,
    done_o
);
parameter BCD_DIGITS_IN_PP    = 2; // # of digits of BCD input
parameter BITS_OUT_PP         = 7; // # of bits of binary output
parameter BIT_COUNT_WIDTH_PP = 3;  // Width of bit counter

```

```

// I/O declarations
input  clk_i;                // clock signal
input  ce_i;                // clock enable input
input  rst_i;               // synchronous reset
input  start_i;             // initiates a conversion
input  [4*BCD_DIGITS_IN_PP-1:0] dat_bcd_i; // input bus
output [BITS_OUT_PP-1:0] dat_binary_o;    // output bus
output done_o;              // indicates conversion is done

reg [BITS_OUT_PP-1:0] dat_binary_o;

// Internal signal declarations

reg [BITS_OUT_PP-1:0] bin_reg;
reg [4*BCD_DIGITS_IN_PP-1:0] bcd_reg;
wire [BITS_OUT_PP-1:0] bin_next;
reg [4*BCD_DIGITS_IN_PP-1:0] bcd_next;
reg busy_bit;
reg [BIT_COUNT_WIDTH_PP-1:0] bit_count;
wire bit_count_done;

//-----
// Functions & Tasks
//-----

function [4*BCD_DIGITS_IN_PP-1:0] bcd_asr;
    input [4*BCD_DIGITS_IN_PP-1:0] din;
    integer k;
    reg cin;
    reg [3:0] digit;
    reg [3:0] digit_more;

begin
    cin = 1'b0;
    for (k=BCD_DIGITS_IN_PP-1; k>=0; k=k-1) // From MS digit to LS digit
    begin
        digit[3] = 1'b0;
        digit[2] = din[4*k+3];
        digit[1] = din[4*k+2];
        digit[0] = din[4*k+1];
        digit_more = digit + 5;
        if (cin)
        begin
            bcd_asr[4*k+3] = digit_more[3];
            bcd_asr[4*k+2] = digit_more[2];
            bcd_asr[4*k+1] = digit_more[1];
            bcd_asr[4*k+0] = digit_more[0];
        end
        else
        begin
            bcd_asr[4*k+3] = digit[3];
            bcd_asr[4*k+2] = digit[2];
            bcd_asr[4*k+1] = digit[1];
            bcd_asr[4*k+0] = digit[0];
        end
        cin = din[4*k+0];
    end
end

```

```

        end // end of for loop
    end

endfunction

//-----
// Module code
//-----

// Perform proper shifting, binary ASL and BCD ASL
assign bin_next = {bcd_reg[0],bin_reg[BITS_OUT_PP-1:1]};
always @(bcd_reg)
begin
    bcd_next <= bcd_asr(bcd_reg);
    // bcd_next <= bcd_reg >> 1; Just for testing...
end

// Busy bit, input and output registers
always @(posedge clk_i)
begin
    if (~rst_i)
    begin
        busy_bit <= 0; // Synchronous reset
        dat_binary_o <= 0;
    end
    else if (start_i && ~busy_bit)
    begin
        busy_bit <= 1;
        bcd_reg <= dat_bcd_i;
        bin_reg <= 0;
    end
    else if (busy_bit && ce_i && bit_count_done && ~start_i)
    begin
        busy_bit <= 0;
        dat_binary_o <= bin_next;
    end
    else if (busy_bit && ce_i & ~bit_count_done)
    begin
        bin_reg <= bin_next;
        bcd_reg <= bcd_next;
    end
end
assign done_o = ~busy_bit;

// Bit counter
always @(posedge clk_i)
begin
    if (~busy_bit) bit_count <= 0;
    else if (ce_i && ~bit_count_done) bit_count <= bit_count + 1;
end
assign bit_count_done = (bit_count == (BITS_OUT_PP-1));

endmodule

```

CRC-serial /parallel implementation

Crc serial:

```
module crc(clk,din,en,rst,out
);
input clk,din,en,rst;
output reg[4:0]out;
wire c1;
assign c1= din ^out[4];
always @(posedge clk)
begin
if(~rst)
out<=0;
else if(en)
begin
out[4]<=out[3];
out[3]<=out[2];
out[2]<=c1^out[1];
out[1]<=out[0];
out[0]<=c1;
end end
endmodule
```

Crc parallel :

```
module crcpar(data,crc_en,rst,clk,crc_out);
input crc_en,rst,clk;
input [7:0]data;
output [4:0]crc_out;
reg [4:0]lfsr_q;
reg [4:0]lfsr_c;
assign crc_out=lfsr_q;
always@(posedge clk)
begin
lfsr_c[0]=lfsr_q[1]^lfsr_q[4]^data[0]^data[3];
lfsr_c[1]=lfsr_q[2]^data[1];
lfsr_c[2]=lfsr_q[1]^lfsr_q[3]^lfsr_q[4]^data[0]^data[2]^data[3];
lfsr_c[3]=lfsr_q[2]^lfsr_q[4]^data[1]^data[3];
lfsr_c[4]=lfsr_q[0]^lfsr_q[3]^data[2];
end
always@(posedge clk)
begin
if(~rst)
begin
lfsr_q<=5'b00000;
end
else if(crc_en)
begin
lfsr_q<=lfsr_c;
//lfsr_q<=crc_en?lfsr_c:lfsr_q;
end
end
endmodule
```


Binary to Bcd

```
module bin_bcd(
    clk_i,
    ce_i,
    rst_i,
    start_i,
    dat_binary_i,
    dat_bcd_o,
    done_o
);
parameter BITS_IN_PP          = 7; // # of bits of binary input
parameter BCD_DIGITS_OUT_PP  = 2;  // # of digits of BCD output
parameter BIT_COUNT_WIDTH_PP = 3;  // Width of bit counter

// I/O declarations
input  clk_i;                // clock signal
input  ce_i;                // clock enable input
input  rst_i;               // synchronous reset
input  start_i;             // initiates a conversion
input  [BITS_IN_PP-1:0] dat_binary_i; // input bus
output [4*BCD_DIGITS_OUT_PP-1:0] dat_bcd_o; // output bus
output done_o;              // indicates conversion is done

reg [4*BCD_DIGITS_OUT_PP-1:0] dat_bcd_o;

// Internal signal declarations

reg [BITS_IN_PP-1:0] bin_reg;
reg [4*BCD_DIGITS_OUT_PP-1:0] bcd_reg;
wire [BITS_IN_PP-1:0] bin_next;
reg [4*BCD_DIGITS_OUT_PP-1:0] bcd_next;
reg busy_bit;
reg [BIT_COUNT_WIDTH_PP-1:0] bit_count;
wire bit_count_done;

//-----
// Functions & Tasks
//-----

function [4*BCD_DIGITS_OUT_PP-1:0] bcd_asl;
    input [4*BCD_DIGITS_OUT_PP-1:0] din;
    input newbit;
    integer k;
    reg cin;
    reg [3:0] digit;
    reg [3:0] digit_less;
    begin
        cin = newbit;
        for (k=0; k<BCD_DIGITS_OUT_PP; k=k+1)
            begin
                digit[3] = din[4*k+3];
                digit[2] = din[4*k+2];
                digit[1] = din[4*k+1];
                digit[0] = din[4*k];
                digit_less = digit - 5;
                if (digit > 4'b0100)

```

```

        begin
            bcd_asl[4*k+3] = digit_less[2];
            bcd_asl[4*k+2] = digit_less[1];
            bcd_asl[4*k+1] = digit_less[0];
            bcd_asl[4*k+0] = cin;
            cin = 1'b1;
        end
    else
        begin
            bcd_asl[4*k+3] = digit[2];
            bcd_asl[4*k+2] = digit[1];
            bcd_asl[4*k+1] = digit[0];
            bcd_asl[4*k+0] = cin;
            cin = 1'b0;
        end
    end // end of for loop
end
endfunction

//-----
// Module code
//-----

// Perform proper shifting, binary ASL and BCD ASL
assign bin_next = {bin_reg,1'b0};
always @(bcd_reg or bin_reg)
begin
    bcd_next <= bcd_asl(bcd_reg,bin_reg[BITS_IN_PP-1]);
end

// Busy bit, input and output registers
always @(posedge clk_i)
begin
    if (~rst_i)
    begin
        busy_bit <= 0; // Synchronous reset
        dat_bcd_o <= 0;
    end
    else if (start_i && ~busy_bit)
    begin
        busy_bit <= 1;
        bin_reg <= dat_binary_i;
        bcd_reg <= 0;
    end
    else if (busy_bit && ce_i && bit_count_done && ~start_i)
    begin
        busy_bit <= 0;
        dat_bcd_o <= bcd_next;
    end
    else if (busy_bit && ce_i && ~bit_count_done)
    begin
        bcd_reg <= bcd_next;
        bin_reg <= bin_next;
    end
end
assign done_o = ~busy_bit;

```

```

// Bit counter
always @(posedge clk_i)
begin
    if (~busy_bit) bit_count <= 0;
    else if (ce_i && ~bit_count_done) bit_count <= bit_count + 1;
end
assign bit_count_done = (bit_count == (BITS_IN_PP-1));
endmodule

```

Hamming code(h,k) encoder /decoder

Encoder:

```

module hamen(clk,d,c
);
input clk;
input [3:0] d;
output reg[6:0] c;
always@(posedge clk)
begin
    c[6]=d[3];
    c[5]=d[2];
    c[4]=d[1];
    c[3]=d[1]^d[2]^d[3];
    c[2]=d[0];
    c[1]=d[0]^d[2]^d[3];
    c[0]=d[0]^d[1]^d[3];
end
endmodule

```

Decoder:

```

module hamd(c,clk,s,c2,d
);
input clk;
input[6:0] c;
output reg[2:0]s;

output reg[6:0] c2;
output reg[3:0]d;

always@(posedge clk)
begin
    s[2]=c[0]^c[4]^c[5]^c[6];
    s[1]=c[1]^c[2]^c[5]^c[6];
    s[0]=c[0]^c[2]^c[4]^c[6];

    c2=c;
    if(s)
    c2[s-1]=~c[s-1];

end
always@(c2)
begin
    d[0]=c2[2];
    d[1]=c2[4];

```

```

d[2]=c2[5];
d[3]=c2[6];
end

endmodule

```

Sequence detector using FSM flow (with output and RTL)

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/////
// Company:
// Engineer:
//
// Create Date:      14:58:32 08/16/2013
// Design Name:
// Module Name:      sequence_0111
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/////
module sequence_0111(clock, reset, in_bit, out_bit
    );

    input clock, reset, in_bit;
    output out_bit;

    reg [2:0] state_reg, next_state;

    // State declaration
    parameter    reset_state = 3'b000;
    parameter    read_zero = 3'b001;
    parameter    read_0_one = 3'b010;
    parameter    read_zero_one_one = 3'b011;
    parameter    read_zero_one_one_one = 3'b100;

    // state register
    always @ (posedge clock or posedge reset)
        if (reset == 1)
            state_reg <= reset_state;
        else
            state_reg <= next_state;

    // next-state logic

```



```

//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////
///

module test_ma_sequence;

    // Inputs
    reg clock;
    reg reset;
    reg in_bit;

    // Outputs
    wire out_bit;

    // Instantiate the Unit Under Test (UUT)
    sequence_0111 uut (
        .clock(clock),
        .reset(reset),
        .in_bit(in_bit),
        .out_bit(out_bit)
    );

    initial begin
        // Initialize Inputs
        clock = 0;
        reset = 0;
        in_bit = 0;

        // Wait 100 ns for global reset to finish
        #10;
        reset = 1;
        in_bit = 0;
        #10;

        reset = 0;
        in_bit = 0;
        #10;

        reset = 0;
        in_bit = 1;
        #10;
        reset = 0;
        in_bit = 1;
        #10;
        reset = 0;
        in_bit = 1;
        #10;
        // Add stimulus here

        reset = 1;
        in_bit = 1;
        #10;
        reset = 0;
    end

```

```

        in_bit = 0;
        #10;
reset = 0;
        in_bit = 1;
        #10;
reset = 0;
        in_bit = 1;
        #10;
reset = 0;
        in_bit = 1;
        #10;
    end
    always begin #5 clock=~clock; end
endmodule

//output waveform

```

